

**Penn State Abington**  
**CMPEN 271**  
**Lecture Set #13**  
**Adders, Multiplication**  
R. Avanzato © 2014-2015

**Topics:**

- Half-adders, Full-adders
- MSI 4-bit ripple adder IC (7483)
- Binary adder applications
  
- Binary Multiplication
  
- Review Questions

**Video part 1 ←**

**Video part 2**

**Video part 3**

# Half-adder

Consider the addition of 2 bits:  $X + Y$



$$\begin{array}{r} X \\ + Y \\ \hline C \quad S \end{array}$$

$$\begin{array}{r} 1 \\ + 1 \\ \hline 1 \quad 0 \\ C \quad S \end{array}$$

X	Y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S \text{ (sum)} = X'Y + XY' = X \oplus Y$$

$$C \text{ (carry)} = XY$$

  


# Full-adder

Consider the addition of 3 bits:  $X + Y + Z$


(inputs)			(outputs)	
<u>X</u>	<u>Y</u>	<u>Z</u>	<u>S(sum)</u>	<u>C(carry)</u>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

```

      Z
      X
    + Y
  -----
  C  S
  
```

 

Block diagram of full-adder

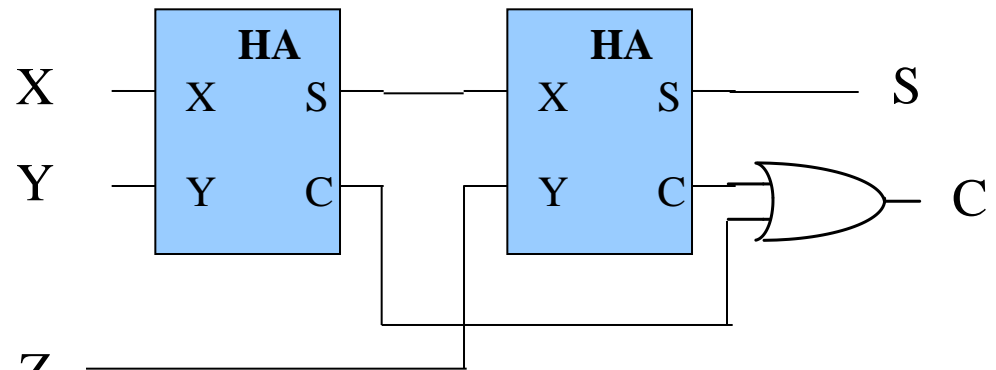

Full-adder from 2 half-adders

$$S \text{ (sum)} = X \oplus Y \oplus Z$$



$$C \text{ (carry)} = XY + Z(X \oplus Y)$$

# 4-bit Binary Adder - 1


What is the best way to implement the following operation?  
(8 inputs, 5 outputs -- could you use truth table and K-map?)

$$\begin{array}{r} A3 \ A2 \ A1 \ A0 \\ + \ B3 \ B2 \ B1 \ B0 \\ \hline S4 \ S3 \ S2 \ S1 \ S0 \end{array}$$

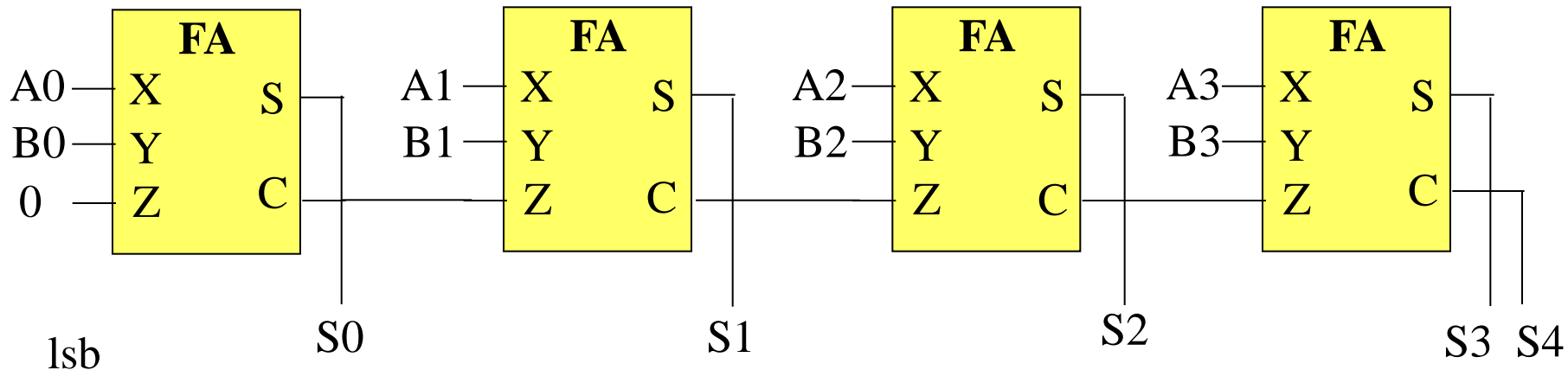 
Add one column  
at a time with a FA.  
Send carry bit to left.



# 4-bit Binary Adder - 2

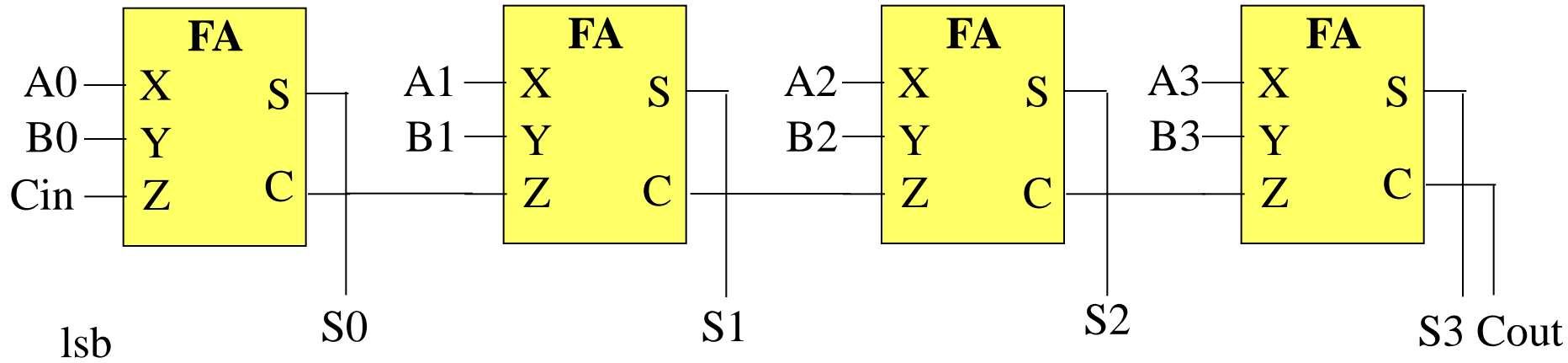

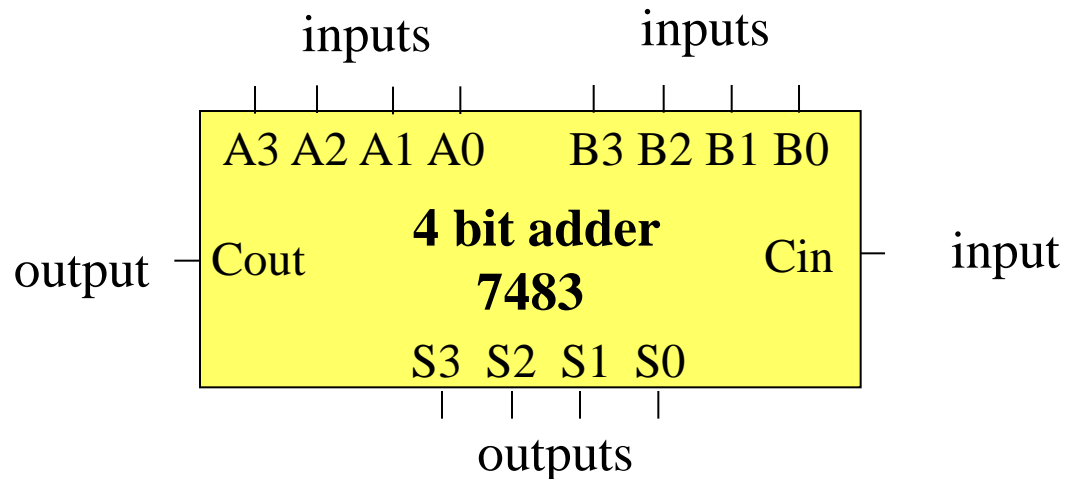
Design engineers  
created the 7483  
4-bit adder MSI chip  
with 4 FAs



# 4-bit Binary Adder - 3

Example: Design a digital circuit which will **add the two, 4-bit numbers  $X_3 X_2 X_1 X_0$  and  $Y_3 Y_2 Y_1 Y_0$** . Use a 7483 4-bit adder in the solution. Determine the number of outputs. Label all inputs and outputs.

Define inputs & outputs:
 
$$\begin{array}{r} X_3 X_2 X_1 X_0 \\ + Y_3 Y_2 Y_1 Y_0 \\ \hline S_4 S_3 S_2 S_1 S_0 \end{array}$$


 
Note difference between internal labels and external labels.

# 4-bit Binary Adder - 4

Example: Design a digital circuit which will **add the two binary numbers X2 X1 X0 and Y1 Y0**. Use a 7483 4-bit adder in the solution. Determine the number of outputs. Label all inputs and outputs.

Define inputs & outputs:

$$\begin{array}{r} X2\ X1\ X0 \\ + \quad Y1\ Y0 \\ \hline S3\ S2\ S1\ S0 \end{array}$$




important - do not leave this input unconnected

# 4-bit Binary Adder - 5

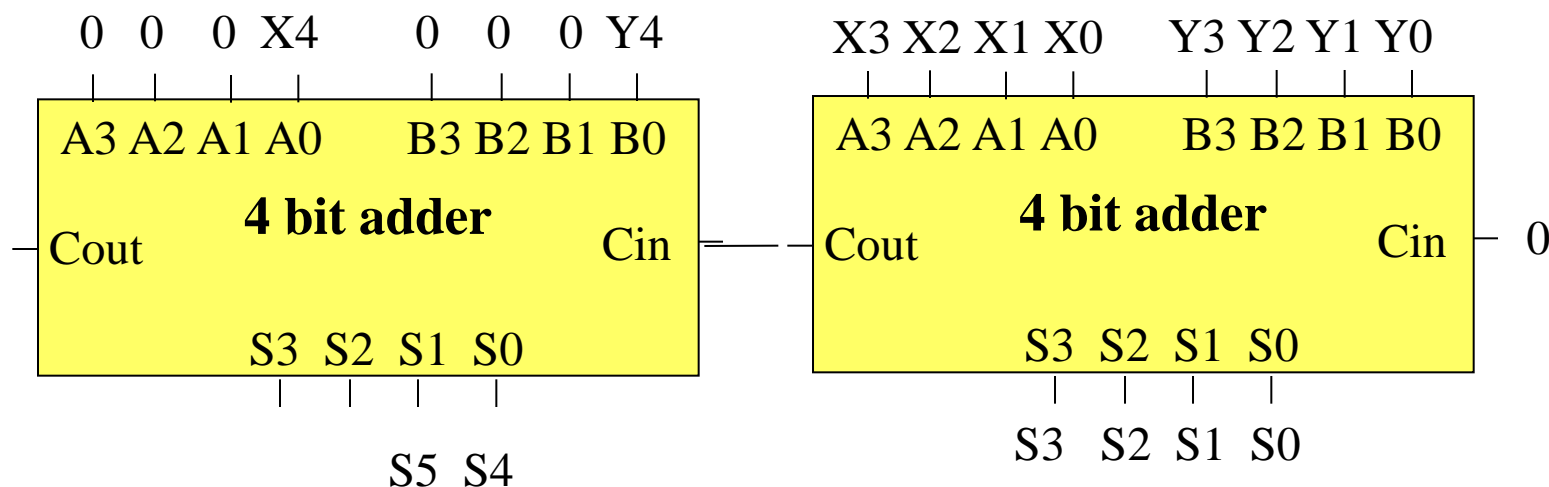Example: Design a digital circuit which will **add the two, 5-bit numbers X4 X3 X2 X1 X0 and Y4 Y3 Y2 Y1 Y0**. Use 7483 4-bit adders in the solution. Determine the number of outputs. Label all inputs and outputs.

Define inputs & outputs:

$$\begin{array}{r} X4\ X3\ X2\ X1\ X0 \\ +\ Y4\ Y3\ Y2\ Y1\ Y0 \\ \hline S5\ S4\ S3\ S2\ S1\ S0 \end{array}$$



Note difference between internal labels and external labels.




# 4-bit Binary Adder - 6

 Example: Design a digital circuit which will **add the value 3 (11) to a 3-bit number X2 X1 X0**. For example if the input is 4 (100) then the output would be 7 (111). Use a 7483 4-bit adder in the solution. Determine the number of outputs. Label all inputs and outputs.

Define inputs & outputs:

$$\begin{array}{r}
 \text{X2 X1 X0} \\
 + \quad \quad 1 \quad 1 \\
 \hline
 \text{S3 S2 S1 S0}
 \end{array}$$




Generalize.

# 4-bit Binary Adder - 7


**Example:** Design a digital circuit which will **increment a 3-bit value, A2 A1 A0, by one**. For example, if the input is 4 (100) then the output would be 5 (101). Use a 7483 4-bit adder in the solution. Determine the number of outputs. Label all inputs and outputs. Show 2 solutions.

Solution #1

 


OR

Solution #2

 


# 4-bit Binary Adder - 8

 **Exercise:** Design a digital circuit which will **add together three, 3-bit numbers** X2 X1 X0, Y2 Y1 Y0, and W2 W1 W0. Use one or more 7483 4-bit adders in the solution. Determine the number of outputs. Label all inputs and outputs.



X2 X1 X0  
Y2 Y1 Y0  
 T3 T2 T1 T0  
W2 W1 W0  
 S4 S3 S2 S1 S0

 - Add 2 numbers at a time; create a temporary result (T3 T2 T1 T0)
- Max output is 21, so 5 bits needed.



# Binary Adders - Summary

- Addition of binary numbers can be accomplished **using truth tables and K-maps OR by using a more modular approach with full adders and 4-bit adder MSI devices**. The truth table approach can be very cumbersome if the number of bits is large. Consider adding 2, 4-bit numbers. The truth table would consist of 256 lines and require minimization of 5, 8-variable functions:

A3	A2	A1	A0	B3	B2	B1	B0	S4	S3	S2	S1	S0	
0	0	0	0	0	0	0	0	0	0	0	0	0	$0 + 0 = 0$
0	0	0	0	0	0	0	1	0	0	0	0	0	$0 + 1 = 1$
0	0	0	0	0	0	1	0	0	0	0	1	0	$0 + 2 = 2$
...								...					
1	1	1	1	1	1	1	1	1	1	1	1	0	$15 + 15 = 30$

- What would be the results if we needed to add 2, 32-bit binary numbers?
- The 4-bit binary adder offers a great deal of flexibility and modularity, and simplifies design.

# Binary Adders - Summary

- 4-bit binary adders (7483 or 74283) can be **cascaded together** to perform addition operations on binary numbers that are greater than 4 bits.
- Binary adders can be relatively **slow** due to the **“ripple” nature** of the carry propagation. For example, in a circuit to add two, 16-bit numbers together, it takes some time for the carry information to propagate through the 16 full adders (from the lsb to the msb). In order to accelerate the addition process, a technique called “lookahead carry” can be used. This circuitry is added to the standard 4-bit binary adder to reduce the delay.  
**Project:** investigate and simulate **“lookahead carry”**. Determine the reduction in time to add 2 binary numbers using lookahead carry. Compare a 4-bit adder with lookahead carry with a 4-bit adder without lookahead carry. [Reference Mano, Kime ,or Wakerly.]

# What you should know about Adders

- Be able to construct truth table and circuit for **half-adder** and **full-adder**.
- Understand and describe **operation and block diagram** (with internal labels) of 7483 4-bit MSI adder.
- Be able to apply 7483 MSI adder to **add any two n-bit binary numbers**. Use appropriate **external labels and internal labels**.
- Be able to **cascade** two or more 7483 MSI adders to solve binary addition problems.

# Penn State Abington

## CMPEN 271

### Lecture Set #13

## Adders, Multiplication

R. Avanzato ©

#### **Topics:**

- Half-adders, Full-adders
- MSI 4-bit ripple adder IC (7483)
- Binary adder applications
- Binary Multiplication
- Review Questions

Video part 1

Video part 2 ←

Video part 3

# Binary Multiplication - 1

Consider a 2-bit x 2-bit multiplication operation.

$$\begin{array}{rcccc}
 & & & A1 & A0 \\
 & & & \times & B1 & B0 \\
 \hline
 & & A1B0 & A0B0 & & \\
 & A1B1 & A0B1 & & & \\
 \hline
 M3 & M2 & M1 & M0 & & 
 \end{array}$$

- 4 inputs A1, A0, B1, B0
- 4 outputs needed.
- What is the max output value?
- Shift and add
- How to produce A0B0 term?
- How do we build a circuit to perform this calculation?


Try some examples.

$$\begin{array}{r}
 10 \\
 \times 11 \\
 \hline
 10 \\
 10 \\
 \hline
 110
 \end{array}$$



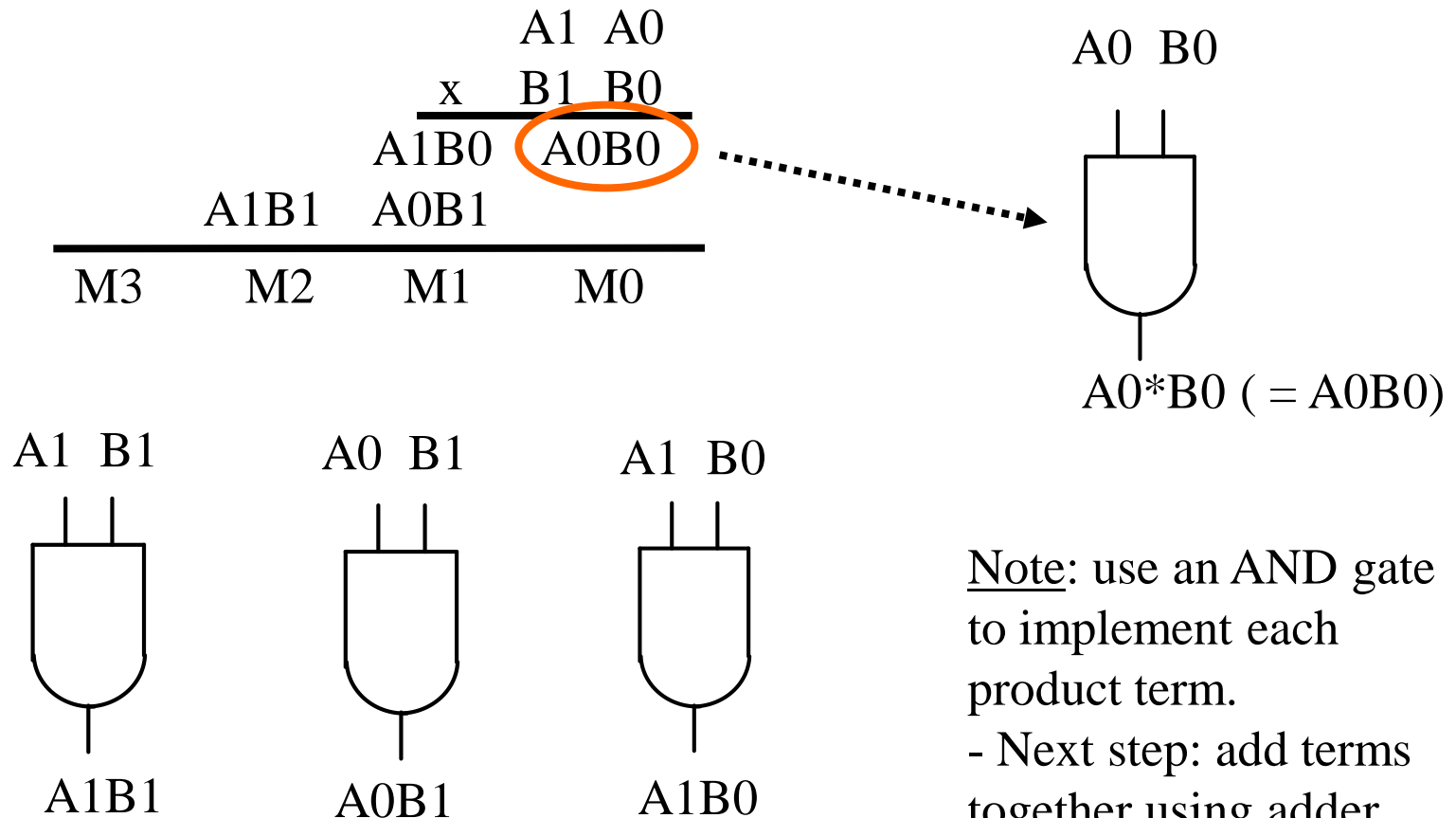
# Binary Multiplication - 2

Consider a 2-bit x 2-bit multiplication operation.



Note: use an AND gate to implement each product term.  
- Next step: add terms together using adder circuit.

# Binary Multiplication - 3

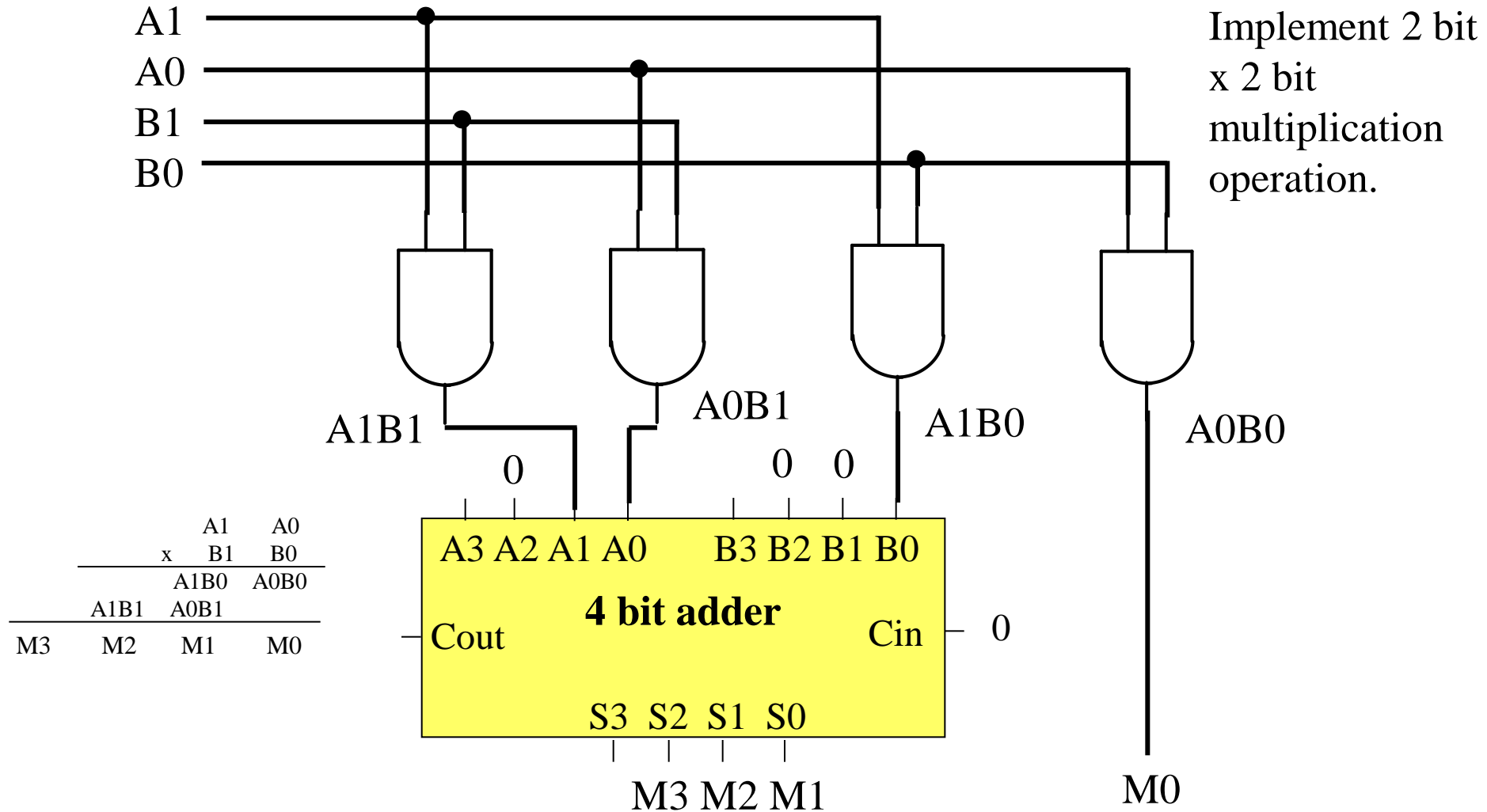

# Binary Multiplication - 4

Consider a 3 bit x 3 bit multiplication operation.

$$\begin{array}{rcccccc}
 & & & & A2 & A1 & A0 \\
 & & & & \times & B2 & B1 & B0 \\
 \hline
 & & & A2B0 & A1B0 & A0B0 \\
 & A2B1 & A1B1 & A0B1 \\
 A2B2 & A1B2 & A0B2 \\
 \hline
 M5 & M4 & M3 & M2 & M1 & M0
 \end{array}$$

- 6 inputs
- 6 outputs needed.
- What is the max output?
- Shift and add
- How to produce A0B0 term?

Try some examples.

$$\begin{array}{r}
 110 \\
 \times 101 \\
 \hline
 \end{array}$$



$$\begin{array}{r}
 111 \\
 \times 111 \\
 \hline
 \end{array}$$

# Binary Multiplication - 5

$$\begin{array}{r}
 \phantom{A2} A2 \ A1 \ A0 \\
 \phantom{A2} \phantom{A1} \times \phantom{A0} B2 \ B1 \ B0 \\
 \hline
 \phantom{A2} A2B0 \phantom{A1B0} A0B0 \\
 \phantom{A2} A2B1 \phantom{A1B1} A0B1 \\
 \phantom{A2} A2B2 \phantom{A1B2} A0B2 \\
 \hline
 M5 \phantom{M4} \phantom{M3} \phantom{M2} \phantom{M1} \phantom{M0} \\
 M4 \phantom{M3} \phantom{M2} \phantom{M1} \phantom{M0} \\
 M3 \phantom{M2} \phantom{M1} \phantom{M0} \\
 M2 \phantom{M1} \phantom{M0} \\
 M1 \phantom{M0} \\
 M0
 \end{array}$$

  Exercise: Design a circuit to perform a 3 bit x 3 bit multiplication operation.

- show calculation
- determine # of outputs
- label all inputs and outputs
- draw circuit.





## Binary Multiplication - 6

$$\begin{array}{r}
 \phantom{x}\phantom{A2}\phantom{A1}\phantom{A0} \\
 \phantom{x}\phantom{A2}\phantom{A1}1\phantom{A0} \\
 \hline
 \phantom{x}A2\phantom{A1}\phantom{A0} \\
 A2\phantom{A1}\phantom{A0} \\
 \hline
 M4\phantom{M3}\phantom{M2}\phantom{M1}\phantom{M0}
 \end{array}$$

  **Exercise:** Design a circuit to multiply a 3-bit number by the constant value of 3 (011)

- show calculation
- 3 inputs only (A2 A1 A0)
- determine # of outputs
- label all inputs and outputs
- draw circuit.
- keep internal labels and external labels separate



# What you should know about binary multiplication

- Be able to design any  $n$ -bit by  $m$ -bit binary multiplier. Show operation, outputs, product terms, label all inputs and outputs, show lsb, circuit, use 4-bit adders where appropriate (Example: 2 by 2, 2 by 3, 3 by 3, 3 by 4, 4 by 4, 4 by 5, etc.)
- Be able to design any  $n$ -bit by constant multiplier. Example: 3-bit (or 4-bit) input multiplied by value of 3 (11) or 5(101) etc. Generalize from examples shown in previous slides.
- Clear documentation, problem statement, sample operation, input labels, output labels for every component are required.
- Can you design a circuit that multiplies a 3-bit number by a constant of 4 (100) without using any gates or components?
- Setup the truth table for a 3-bit by 3-bit multiplier. What is the disadvantage of this approach? How many IC's are required?

# Practice Exercises

- Design circuit to **add** two, 3-bit numbers (A2,A1,A0; B2; B1, B0) with a 7483 adder chip. Label all inputs and outputs.
- Design circuit to **add** two 6-bit binary numbers with one or more 7483 adder chip(s). Label all inputs and outputs.
- Design circuit to **multiply** a 3-bit number by a 2 bit number (future HW problem)
- Design a circuit to **multiply** a 4-bit binary number by the constant 5.
- Design a circuit to **multiply** a 4-bit binary number by the constant 4. (do not use any gates!)

# Summary

- The **4-bit binary adder** (7483) is an MSI device and it incorporates 4 full adders internally. It can be used as a building block to design complex circuits.
- The 4-bit adder can **add two, 4-bit binary numbers** (8 data inputs). There are 4 outputs plus a carry out. There is also a carry-in input.
- The **7483 IC can be cascaded** to perform addition of larger binary numbers. For example, one 7483 can add two, 4-bit numbers; two 7483 chips can add two, 8-bit numbers and so on. The carry-out of one 7483 must be connected to the carry-in of the next 7483 chip in the appropriate fashion.
- A 4-bit adder (such as the 7483) is generally represented by a **block diagram showing internal labels** for all inputs and outputs.
- **Binary multiplication** is implemented using AND gates to perform the bit multiplication, and one or more MSI adder chips to add the results.
- When designing digital circuits to perform addition and multiplication of binary numbers, it is important to **clearly define all inputs and all outputs**. Generally the inputs will be defined in the problem, but you must determine how many outputs will be generated and provide the outputs with appropriate labels/names (and also clearly define lsb, msb)



# Further Reading

- Mano, Kime, Logic and Computer Design Fundamentals, 2nd edition, Prentice Hall (Chapter 3).

# Penn State Abington

## CMPEN 271

### Lecture Set #13

## Adders, Multiplication

R. Avanzato ©

#### **Topics:**

- Half-adders, Full-adders
- MSI 4-bit ripple adder IC (7483)
- Binary adder applications

Video part 1

- Binary Multiplication


Video part 2

- Review Questions

Video part 3 ←

# Sample Questions
 
#1.- What are the outputs of the following 4-bit adder circuit?



- a)  $C_{out} = 0; S_3=0; S_2=0; S_1=1; S_0=1$       b)  $C_{out} = 0; S_3=0; S_2=0; S_1=1; S_0=0$   
c)  $C_{out} = 1; S_3=0; S_2=0; S_1=1; S_0=0$       d)  $C_{out} = 1; S_3=0; S_2=0; S_1=1; S_0=1$

# Sample Questions

#2.- What are the outputs of the following 4-bit adder circuit?



- a)  $C_{out} = 1; S_3=1; S_2=1; S_1=1; S_0=1$     b)  $C_{out} = 1; S_3=0; S_2=0; S_1=1; S_0=0$   
c)  $C_{out} = 1; S_3=0; S_2=0; S_1=1; S_0=1$     d)  $C_{out} = 1; S_3=1; S_2=1; S_1=1; S_0=0$

# Sample Questions

#3.- How many outputs are required for a circuit that multiplies 2, 2-bit numbers?

- a) 2      b) 3      c) 4      d) 5      e) 6

#4.- How many outputs are required for a circuit that multiplies 2, 3-bit numbers?

- a) 2      b) 3      c) 4      d) 5      e) 6