

CMPEN 271 Final Exam Practice Questions (with solutions)
 Bob Avanzato, Penn State Abington, rla5@psu.edu, copyright 2009-2010
 Version 1.9 (6-3-2017) Note: Be able to GENERALIZE!! Ask questions.
Note: Choice "a" is the correct answer for each question

Part 1: D FFs, shift registers and ring counters (Lecture #16)

Part 2: JK FFs; ripple counters (Lecture #17)

Part 3: Finite State Machines (FSM) with D Flip Flops (Lecture #18)

Part 4: State Machines with JK Flips flops and Applications Lecture #19)

Part 5: MSI Counters and MSI Shift Registers (Lecture #20)

Part 6: Memory Concepts (Lecture #21)

Part 1: D FFs, shift registers and ring counters

1.1.- How many bits are stored in a single D flip flop?

- a) 1 b) 2 c) 3 d) 4


1.2.-When a flip-flop is "set", then the outputs of the flip-flop are

- a) $Q=1, Q'=0$ b) $Q=0, Q'=1$ c) $Q=0, Q'=0$ d) $Q=1, Q'=1$

1.3.-When a flip-flop is "reset" or "cleared", then the outputs of the flip-flop are


- a) $Q=0, Q'=1$ b) $Q=1, Q'=0$ c) $Q=0, Q'=0$ d) $Q=1, Q'=1$

 1.4.- What is the output of this D flip-flop below after 1 clock pulse?



- a) $Q=0, Q'=1$ b) $Q=0, Q'=0$ c) $Q=1, Q'=0$ d) $Q=1, Q'=1$

 1.5.- What is the output of this D flip-flop below after 1 clock pulse?



- a) $Q=0, Q'=1$ b) $Q=0, Q'=0$ c) $Q=1, Q'=0$ d) $Q=1, Q'=1$

1.6.- A 3-bit shift register has how many D flip-flops?

- a) 3 b) 4 c) 6 d) 8


1.7.- A 3-bit ring counter has how many D flip-flops?

- a) 3 b) 4 c) 6 d) 8


1.8.- A digital circuit which contains at least one flip-flop is called a(n)

- a) sequential circuit b) combinational circuit c) analog circuit

 
1.9.- Fill in the waveform which describes the output Q of a positive-edge triggered D flip-flop




(answer)

 

 
1.10.- Fill in the waveform which describes the output Q of a negative-edge triggered D flip-flop



Answer:

 

 
1.11.- Consider the shift register below. Assume all FFs are initially set to 0.



What are the FF outputs after 1 clock pulse?

- a) $QA=1, QB=0, QC=0$
- b) $QA=0, QB=0, QC=0$
- c) $QA=1, QB=1, QC=0$
- d) $QA=1, QB=1, QC=1$

 
1.12.- Consider the shift register circuit below. Assume all FFs are initially set to 0.



1.13.- What are the FF outputs after 2 clock pulses?

- a) $QA=1, QB=1, QC=0$
- b) $QA=0, QB=0, QC=0$
- c) $QA=1, QB=1, QC=0$
- d) $QA=1, QB=1, QC=1$

 
1.14.- Consider the shift register circuit below. Assume all FFs are initially set to 0.



What are the FF outputs after 10 clock pulses?

- a) $QA=1, QB=1, QC=1$
- b) $QA=0, QB=0, QC=0$
- c) $QA=0, QB=1, QC=0$
- d) $QA=0, QB=1, QC=1$

 
1.15.- Consider the shift register circuit below. Assume all FFs are initially set to 1.



What are the FF outputs after 2 clock pulses?

- a) $QA=0, QB=0, QC=1$ b) $QA=1, QB=1, QC=0$
 c) $QA=0, QB=1, QC=1$ d) $QA=0, QB=1, QC=1$

 
1.16.- Consider the ring counter below. Assume initially $QA=1, QB=0, QC=0$.



What are the FF outputs after 1 clock pulse?

- a) $QA=0, QB=1, QC=0$ b) $QA=0, QB=0, QC=0$
 c) $QA=1, QB=0, QC=0$ d) $QA=1, QB=1, QC=1$

 
1.17.- Consider the ring counter below. Assume initially $QA=1, QB=0, QC=0$.



What are the FF outputs after 3 clock pulses?

- a) $QA=1, QB=0, QC=0$ b) $QA=0, QB=1, QC=0$
 c) $QA=0, QB=0, QC=1$ d) $QA=1, QB=1, QC=1$

 
1.18.- Consider the “twisted” ring counter below. Assume initially $QA=1, QB=0, QC=0$.



What are the FF outputs after 1 clock pulse?

- a) $QA=1, QB=1, QC=0$ b) $QA=0, QB=0, QC=0$
 c) $QA=1, QB=0, QC=0$ d) $QA=1, QB=1, QC=1$

 1.19.- Consider the “twisted” ring counter below. Assume initially $QA=1, QB=0, QC=0$.




1.20.- What are the FF outputs after 2 clock pulses?

- a) $QA=1, QB=1, QC=1$ b) $QA=0, QB=0, QC=0$
 c) $QA=1, QB=1, QC=0$ d) $QA=1, QB=1, QC=1$

1.21.- A digital circuit which contains no flip-flop or memory elements is called a(n)
 a) combinational circuit b) sequential circuit c) analog circuit

 
1.22.- Consider the ring counter circuit below. Assume initially $QA=1, QB=0, QC=0$.



How would you describe the behavior of the motor output M?

- a) M is on for 2 seconds, off for 1 second, then repeat
 b) M is on for 3 seconds, off for 1 second, then repeat
 c) M is on for 1 second, off for 2 seconds, then repeat
 d) M is always on
 e) M is always off

 1.23.- Consider the ring counter circuit below. Assume initially $QA=1$, $QB=1$, $QC=0$.



How would you describe the behavior of the motor output M? (Be careful with initial conditions)

- a) M is always on
- b) M is on for 2 seconds, off for 1 second, then repeat
- c) M is on for 3 seconds, off for 1 second, then repeat
- d) M is on for 1 second, off for 2 seconds, then repeat
- e) M is always off

Part 2: JK FFs; ripple counters

2.1.- How many bits are stored in a single JK flip flop?

- a) 1 b) 2 c) 3 d) 4

2.2.- To place a JK flip-flop in "toggle" mode, the data inputs should be

- a) J=1, K=1 b) J=0, K=0 c) J=0, K=1 d) J=1, K=0

2.3.- To "set" a JK flip-flop, the inputs should be (assuming initial Q is unknown)

- a) J=1, K=0 b) J=0, K=0 c) J=0, K=1 d) J=1, K=1

2.4.- To "reset" or "clear" a JK flip-flop, the inputs should be (assuming initial Q is unknown)

- a) J=0, K=1 b) J=0, K=0 c) J=1, K=0 d) J=1, K=1

2.5.- If J=1 and K=1 for a JK flip-flop and the initial Q = 0, what are the outputs after one clock pulse?

- a) Q = 1, Q' = 0 b) Q = 0, Q' = 0 c) Q = 1, Q' = 1 d) Q = 0, Q' = 1

2.6.- If J=1 and K=1 for a JK flip-flop and the initial Q = 0, what is output after two clock pulses?

- a) Q = 0, Q' = 1 b) Q = 0, Q' = 0 c) Q = 1, Q' = 1 d) Q = 1, Q' = 0

2.7.- A 3-bit ripple counter uses how many JK flip-flops?

- a) 3 b) 2 c) 4 d) 8

2.8.- A 3-bit ripple counter has a count sequence of

- a) 0 to 7 b) 0 to 8 c) 0 to 3 d) 1 to 4

2.9.- A 3-bit ripple counter is also known as a

- a) MOD-8 counter b) MOD-4 counter c) MOD-3 counter d) MOD-16 counter

2.10.- A 3-bit ripple counter is also known as a

- a) divide-by-8 counter b) divide-by-4 counter c) divide-by-3 counter
d) divide-by-16 counter

2.11.- A MOD-9 ripple counter has a count sequence of


- a) 0 to 8 b) 0 to 9 c) 0 to 3 d) 0 to 10

2.12.- A MOD-9 ripple counter requires how many JK flip-flops?

- a) 4 b) 3 c) 2 d) 5

 
- 2.13.- When you design a MOD-9 ripple counter with JK flips-flops, at what number do you active the reset for all of the flip-flops?
 a) 9 b) 8 c) 10 d) 11 e) 16
- 2.14.- If the clock input to a 3-bit ripple counter is 1KHz, then the frequency of the lsb of the counter is
 a) 500Hz b) 1KHz c) 250Hz d) 125Hz
- 2.15.- If the clock input to a 3-bit ripple counter is 1KHz, then the frequency of the msb of the counter is
 a) 125Hz b) 1KHz c) 250Hz d) 500Hz
- 2.16.- If the clock input to a 5-bit ripple counter is 32 KHz, then the frequency of the lsb of the counter is
 a) 16Hz b) 32KHz c) 1KHz d) 500Hz
- 2.17.- If the clock input to a 5-bit ripple counter is 32 KHz, then the frequency of the msb of the counter is
 a) 1KHz b) 8KHz c) 16KHz d) 32KHz
- 2.18.- A ripple counter is a(n) _____ circuit.
 a) asynchronous b) synchronous c) combinational d) MSI

Consider the ripple counter circuit below



 - 2.19.- What is the MOD of the ripple counter above?
 a) MOD 4 b) MOD 2 c) MOD 3 d) MOD 8
- 2.20.- What is the count sequence of the ripple counter above?
 a) 0 to 3 b) 1 to 4 c) 1 to 3 d) 0 to 7 e) 0 to 1
- 2.21.- How many states does the ripple counter above contain?
 a) 4 b) 2 c) 3 d) 5 e) 8
- 2.22.- What is the least significant bit of the ripple counter above?
 a) A b) B
- 2.23.- What is the most significant bit of the counter above?
 a) B b) A

Consider the ripple counter circuit below:



2.24.- How many FFs are contained in the circuit above?

- a) 3 b) 2 c) 4 d) 8

2.25.- What is the MOD of the ripple counter above?

- a) MOD 5 b) MOD 2 c) MOD 3 d) MOD 8

2.26.- What is the count sequence of the ripple counter above?

- a) 0 to 4 b) 1 to 4 c) 1 to 5 d) 0 to 5 e) 0 to 1

2.27.- How many states does the ripple counter above contain?

- a) 5 b) 2 c) 4 d) 6 e) 8

2.28.- What is the least significant bit of the ripple counter above?

- a) A b) B c) C

2.29.- What is the most significant bit of the counter above?

- a) C b) A c) B

2.30.- A MOD-50 ripple counter has a count sequence of

- a) 0 to 49 b) 0 to 50 c) 1 to 49 d) 0 to 5

2.31.- A MOD-50 ripple counter has how many JK flip-flops?

- a) 6 b) 5 c) 4 d) 7 e) 50

2.32.- If you want to design a ripple counter with a count sequence of 0 to 75, on what count would you reset all of the FFs to zero?

- a) 76 b) 74 c) 75 d) 73


2.33.- A ripple counter with a count sequence of 0 to 75 would correspond to what MOD?

- a) 76 b) 74 c) 75 d) 77


2.34.- Ripple counters are referred to as “asynchronous” circuits because...

- a) not every JK flip-flop is connected directly to the master clock
b) each JK flip-flop has a reset input
c) each JK flip-flop is in toggle mode

 
2.35.- Fill in the waveform for the output Q of a negative-edge triggered FF




(answer)

 

 2.36.- Fill in the waveform for the output Q of a negative-edge triggered FF



(answer)

 

Part 3: Finite State Machines (FSM)


3.1 A “synchronous” circuit means that every FF in the circuit is
a) directly connected to master clock b) a D FF c) is a JK FF d) has a reset
e) is positive-edge triggered

3.2 Every sequential circuit is synchronous.
a) false b) true

3.3 Every synchronous circuit is sequential.
a) true b) false

3.4 A state machine is a(n) _____ circuit.
a) synchronous b) asynchronous c) combinational d) analog

 3.5 Consider the following state diagram.




3.6 How many states are represented in the state diagram above?
a) 3 b) 1 c) 2 d) 5

3.8. How many FFs (minimum) would be required to implement the state diagram above?
a) 2 b) 1 c) 3 d) 4

3.9 How many external inputs are represented in the state diagram above?
a) 0 b) 1 c) 2 d) 3


3.10 How many unused states are represented in the state diagram above?
a) 1 b) 0 c) 2 d) 3

Consider the following state diagram:

 


- 3.11 How many states are represented in the state diagram above?
 a) 4 b) 1 c) 2 d) 3 e) 5
- 3.12 How many FFs (min) would be required to implement the state diagram above?
 a) 2 b) 1 c) 3 d) 4
- 3.13 How many external inputs are represented in the state diagram above?
 a) 0 b) 1 c) 2 d) 3
- 3.14 How many unused states are represented in the state diagram above?
 a) 0 b) 1 c) 2 d) 3
- 3.15 What is the FF input equation DA represented in the state diagram above?
 a) $DA = B$ b) $DA = A$ c) $DA = AB$ d) $DA = 0$ e) $DA = 1$
- 3.16 What is the FF input equation DB represented in the state diagram above?
 a) $DB = A'$ b) $DB = A$ c) $DB = B$ d) $DB = 0$ e) $DB = 1$

Consider the following state diagram:

 

- 3.17 How many external inputs are represented in the state diagram above?
 a) 1 b) 0 c) 2 d) 3
- 3.18 Assume initially $A=1, B=1$. What is value of A, B after 3 clock pulses? Let input $E=1$.
 a) $A=0, B=1$ b) $A=0, B=0$ c) $A=1, B=0$ d) $A=1, B=1$
- 3.19 Assume initially $A=1, B=0$. What is value of A, B after 3 clock pulses? Let input $E=0$.
 a) $A=1, B=0$ b) $A=0, B=0$ c) $A=0, B=1$ d) $A=1, B=1$

Consider the state machine below:

 

3.20 What is the flip-flop equation for flip-flop A?

- a) $DA = AB$ b) $DA = A'$ c) $DA = \text{Clock}$ d) $DA = A$

3.21 What is the flip-flop equation for flip-flop B?

- a) $DB = A'$ b) $DA = AB$ c) $DB = \text{Clock}$ d) $DB = A$

3.22 Draw the state table for state machine circuit above.

a) P. S. N. S.


| A | B | A | B |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 |

b) P. S. N. S.


| A | B | A | B |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 |

3.23 Draw the state table for state machine circuit above.


a)

 

b)

 





c)

 

Consider the state table below

| P.S. | | N.S. | |
|----------|----------|----------|----------|
| <u>A</u> | <u>B</u> | <u>A</u> | <u>B</u> |
| 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 |

    3.24 Choose the state diagram which corresponds to the state table above:



3.25 What are the FF input equations for the state table above?

a) $DA = A'B$; $DB = A'B'$

c) $DA = AB'$; $DB = 0$

b) $DA = A'B'$; $DB = A'B$

d) $DA = 0$; $DB = A'B$

Part 4: FSM with JK Flip Flops and Applications

Consider the following state table for a FSM using JK flip-flops

| <u>Present State</u> | | <u>Next State</u> | | <u>FF input eq's</u> | | | |
|----------------------|----------|-------------------|----------|----------------------|-----------|-----------|-----------|
| <u>A</u> | <u>B</u> | <u>A</u> | <u>B</u> | <u>JA</u> | <u>KA</u> | <u>JB</u> | <u>KB</u> |
| 0 | 0 | 0 | 1 | 0 | X | 1 | X |
| 0 | 1 | 1 | 0 | 1 | X | X | 1 |
| 1 | 0 | 1 | 1 | X | 0 | 1 | X |
| 1 | 1 | 0 | 0 | X | 1 | X | 1 |

3.26 How many flip-flops are represented in above state diagram?

- a) 2 b) 3 c) 4 d) 5


3.27 What is the flip-flop input equation for flip-flop A?

- a) $JA=B, KA=B$ b) $JA=AB, KA=B$ c) $JA=0, KA=B$ d) $JA=1, KA=1$

3.28 What is the flip-flop input equation for flip flop B?

- a) $JB=1, KB=1$ b) $JB=A, KB=B$ c) $JB=0, KB=B$ d) $JB=A, KB=1$

 3.29 Consider the state machine below designed with JK flip-flops?




3.20 What is the flip-flop input equation for flip-flop A?


- a) $JA=B, KA=B$ b) $JA=AB, KA=B$ c) $JA=0, KA=B$ d) $JA=1, KA=1$

3.21 What is the flip-flop input equation for flip flop B?


- a) $JB=1, KB=1$ b) $JB=A, KB=B$ c) $JB=0, KB=B$ d) $JB=A, KB=1$

 3.22 Draw the state diagram for the circuit above



 

 Consider the following state diagram for a binary sequence detector.




- 3.23 In the state machine form above, the notation “x/y” denotes
- x is an input and y is an output
 - x is an input and y is an input
 - x is an output and y is an output
 - x is divided by y
- 3.24 What does the symbol “0/1” mean in a state diagram?
- if the input = 0 then set the output = 1 and make the state transition
 - if the input = 1 then set the output = 0 and make the state transition
 - if the input = 0 then set the output = 0 and make the state transition
- 3.25 What does the symbol “1/0” mean in a state diagram?
- if the input = 1 then set the output = 0 and make the state transition
 - if the input = 0 then set the output = 1 and make the state transition
 - if the input = 0 then set the output = 0 and make the state transition
- 3.26 What binary sequence is detected in the FSM above? That is, starting at state A, what sequence of bits will produce an output of 1?
- 101
 - 111
 - 1011
 - 0100
 - 110
- 3.27 Initially the state machine is in state A. What is the output of this circuit if the input sequence = 001010 ?
- 000010
 - 001010
 - 000011
 - 000111
- 3.28 Initially the state machine is in state A. What is the output of this circuit if the input sequence = 00000 ?
- 00000
 - 00101
 - 000011
 - 000111
- 3.29 Initially the state machine is in state A. What is the output of this circuit if the input sequence = 11111 ?
- 00000
 - 11111
 - 000011
 - 000111
- 3.20 Initially the state machine is in state A. What is the output of this circuit if the input sequence = 10110101
- 00100100
 - 00100000
 - 11111101
 - 00000010
- 3.21 How many states does the state diagram for the sequence detector above contain?
- 3
 - 2
 - 4
 - 5
 - 6

3.22 How many flip-flops (minimum) are necessary to implement the circuit above?

- a) 2 b) 1 c) 3 d) 4 e) 8

 Part 5: MSI Counters and MSI Shift Registers

Consider the following circuit (fig. 4.0)



4.1 What type of MSI device is depicted above (fig 4.0)?

- a) register b) counter c) decoder d) multiplexer e) ripple counter


4.2 How many flip-flops are contained within the device above (fig 4.0)?

- a) 4 b) 2 c) 3 d) 5 e) 8

4.3 How many bits are stored in the device above (fig 4.0)?

 - a) 4 b) 2 c) 3 d) 5 e) 8

Given the bi-directional shift register below (fig 4.1),



4.3 How many flip-flops are contained in the device above (fig 4.1)?

- a) 4 b) 3 c) 5 d) 6 e) 8

4.5 In Fig. 4.1, assume initially $Q3 = Q2 = Q1 = Q0 = 0$, $S1=0$ and $S0=1$, and $SR = 1$, then what are the outputs after one clock pulse?

- a) $Q3=1, Q2=0, Q1=0, Q0=0$ b) $Q3=1, Q2=1, Q1=0, Q0=0$
c) $Q3=0, Q2=0, Q1=0, Q0=0$ d) $Q3=1, Q2=1, Q1=1, Q0=1$

4.6 In Fig. 4.1, assume initially $Q_3 = Q_2 = Q_1 = Q_0 = 0$, $S_1 = 0$ and $S_0 = 1$, and $SR = 1$, then what are the outputs after two clock pulses?

- a) $Q_3 = 1, Q_2 = 1, Q_1 = 0, Q_0 = 0$
- b) $Q_3 = 1, Q_2 = 0, Q_1 = 0, Q_0 = 0$
- c) $Q_3 = 0, Q_2 = 0, Q_1 = 0, Q_0 = 0$
- d) $Q_3 = 1, Q_2 = 1, Q_1 = 1, Q_0 = 1$

4.7 In Fig. 4.1, assume initially $Q_3 = Q_2 = Q_1 = Q_0 = 0$, $S_1 = 0$ and $S_0 = 0$, and $SR = 1$, then what are the outputs after two clock pulses (fig. 1)?

- a) $Q_3 = 0, Q_2 = 0, Q_1 = 0, Q_0 = 0$
- b) $Q_3 = 1, Q_2 = 0, Q_1 = 0, Q_0 = 0$
- c) $Q_3 = 1, Q_2 = 1, Q_1 = 0, Q_0 = 0$
- d) $Q_3 = 1, Q_2 = 1, Q_1 = 1, Q_0 = 1$

4.8 In Fig. 4.1, assume initially $Q_3 = Q_2 = Q_1 = Q_0 = 0$, $S_1 = 1$ and $S_0 = 0$, and $SL = SR = 1$, then what are the outputs after two clock pulses (fig. 1)?


- a) $Q_3 = 0, Q_2 = 0, Q_1 = 1, Q_0 = 1$
- b) $Q_3 = 1, Q_2 = 0, Q_1 = 0, Q_0 = 0$
- c) $Q_3 = 1, Q_2 = 1, Q_1 = 0, Q_0 = 0$
- d) $Q_3 = 1, Q_2 = 1, Q_1 = 1, Q_0 = 1$

4.9 In Fig. 4.1, assume initially $Q_3 = Q_2 = Q_1 = Q_0 = 1$, $S_1 = 0$ and $S_0 = 1$, and $SL = SR = 0$, then what are the outputs after two clock pulses (fig. 1)?

- a) $Q_3 = 0, Q_2 = 0, Q_1 = 1, Q_0 = 1$
- b) $Q_3 = 1, Q_2 = 0, Q_1 = 0, Q_0 = 0$
- c) $Q_3 = 1, Q_2 = 1, Q_1 = 0, Q_0 = 0$
- d) $Q_3 = 1, Q_2 = 1, Q_1 = 1, Q_0 = 1$

Consider the MSI 74163 counter below (fig 4.2)

74163 MSI Counter

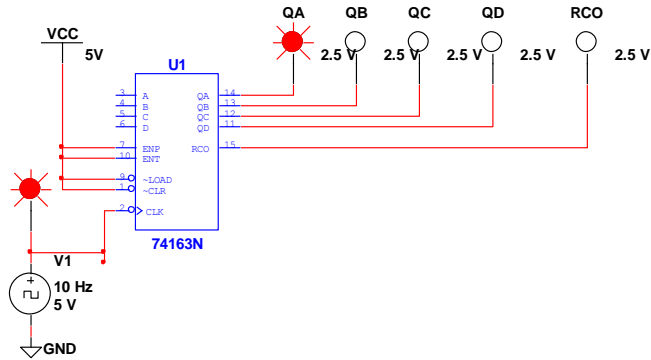

4.10 How many flip-flops are contained within the MSI counter above?

- a) 4 b) 2 c) 3 d) 5


4.11 What is the count sequence of the circuit above (fig. 4.2)?

- a) 0 to 15 b) 0 to 4 c) 0 to 16 d) 1 to 15 e) 0 to 31

4.12 What is the MOD of the counter above (fig. 4.2)?

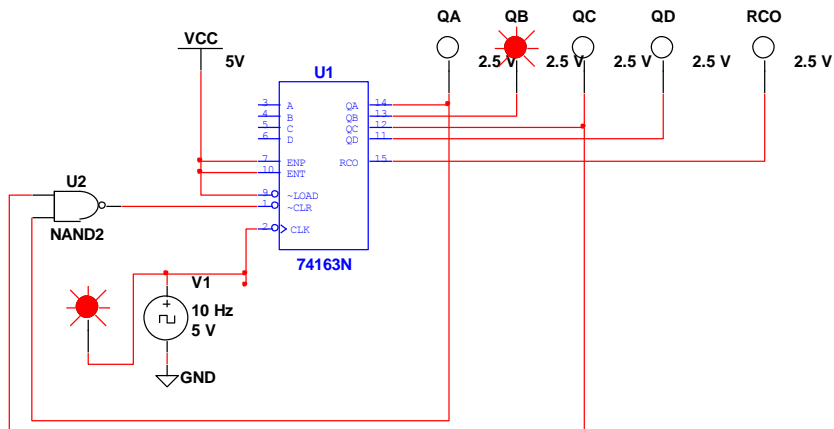- a) MOD 16 b) MOD 15 c) MOD 4 d) MOD 8

Consider the MSI 74163 counter circuit diagram below (fig. 4.3)



- 4.13 How many flip-flops are contained within the MSI counter above (fig. 4.3)?
a) 4 b) 2 c) 3 d) 5
- 4.14 What is the count sequence of the circuit above (fig. 4.3)?
a) 0 to 5 b) 0 to 4 c) 0 to 6 d) 1 to 15 e) 0 to 7
- 4.15 What is the MOD of the counter above (fig. 4.3)?
a) MOD 6 b) MOD 4 c) MOD 5 d) MOD 8
- 4.16 If you want to design a MOD-10 counter with a 74163 counter, at what count value do you activate the flip flop clear?
a) 9 b) 8 c) 10 d) 11 e) 16
- 4.17 In general, a 16-bit register has how many flip-flops?
a) 16 b) 8 c) 4 d) 2
- 4.18 In general, a 16-bit register can store how many bits?
a) 16 b) 8 c) 4 d) 2

Part 6: Memory Concepts

5.1 The term "RAM" means

- a) random access memory b) radix arithmetic memory
- c) random average memory d) raster access machine

5.2 The term "ROM" means

- a) read-only memory b) random-only memory
- c) read-often memory d) reset-only memory

5.3 The term "DRAM" means

- a) dynamic RAM b) differential RAM c) D flip-flop RAM d) digital RAM

5.4 The term "SRAM" means

- a) static RAM b) sonic RAM c) standard RAM d) synchronous RAM

5.5 The term "EPROM" means

- a) erasable ROM b) electric ROM c) energy ROM d) entropy ROM

5.6 Flash memory is a type of

- a) EEPROM b) SRAM c) DRAM d) EPROM

5.7 RAM memory is

- a) volatile b) non-volatile

5.8 ROM memory is

- a) non-volatile b) volatile

5.9 EEPROM memory is

- a) non-volatile b) volatile

5.10 Flash memory is

- a) non-volatile b) volatile

5.11 EPROM memory is

- a) non-volatile b) volatile

5.12 SRAM memory is

- a) volatile b) non-volatile

5.13 DRAM memory is

- a) volatile b) non-volatile

5.14 Cache memory is generally of what type?

- a) SRAM b) DRAM c) ROM d) PROM

- 5.15 The storage unit of SRAM consists of a(n)
a) flip-flop b) capacitor c) inductor d) electron
- 5.16 The storage unit of DRAM consists of a(n)
a) capacitor b) flip-flop c) inductor d) electron
- 5.17 Which memory technology uses UV light to erase its contents?
a) EPROM b) EEPROM c) Flash d) RAM
- 5.18 How many address lines are required for a 1Kx8 memory module?
a) 10 b) 8 c) 9 d) 1024
- 5.19 How many data lines are required for a 1Kx8 memory module?
a) 8 b) 9 c) 10 d) 16
- 5.20 How many address lines are required for a 64x16 memory module?
a) 6 b) 8 c) 9 d) 1
- 5.21 How many data lines are required for a 64x16 memory module?
a) 16 b) 6 c) 10 d) 8
- 5.22 How many address lines are required for a 16Kx8 memory module?
a) 14 b) 8 c) 16 d) 10
- 5.23 How many data lines are required for a 16Kx8 memory module?
a) 8 b) 9 c) 10 d) 16
- 5.24 A tri-state (or 3-state) output means
a) the output is either logic 0, logic 1, or high impedance (Z)
b) the output is a voltage between 0v and 5 v
c) there are 3 outputs
- 5.25 Tri-state logic supports
a) communication on a common bus
b) driving high current devices
c) high frequency counters