

CMPEN 271 Exam #2 Practice Problems v3

Part 2: MSI Devices; Multiplexers, Decoder, Adders, Magnitude Comparators; Addition; Multiplication; Signed Number Systems; HDL; Latches

R. Avanzato © 2014-2017

Note: correct answer is choice “a” for every question

Contents:

Part 1. MSI Devices (Decoders, Encoders, MUXs, Magn. Comp., Adders)
(Lectures #11-13)

Part 2. Signed Number Systems (Lecture #14)

Part 3. HDL (Lecture #15)

Part 4. SR (NAND, NOR) Latches (Lecture #15)

Part 1. MSI Devices

A decoder is a(n)

- a) MSI device b) logic gate c) flip-flop d) number system

A 3x8 decoder has how many “data” inputs?

- a) 3 b) 1 c) 2 d) 8

A 3x8 decoder has how many “data” outputs?

- a) 8 b) 1 c) 2 d) 3

A decoder can be used to

- a) implement Boolean functions b) store information c) minimize Boolean functions
d) create K-maps

A 4x16 decoder has how many data inputs?

- a) 4 b) 1 c) 2 d) 16

A 4x16 decoder has how many data outputs?

- a) 16 b) 4 c) 1 d) 2

Which of the following is an application of an encoder?

- a) keyboard circuit b) adder c) subtractor d) demultiplexer

A 4x16 decoder can be constructed from

- a) two 3x8 decoders b) two 2x4 decoders c) two 1x2 decoders d) two 4x1
multiplexers

A multiplexer is a(n)

- a) MSI device b) logic gate c) flip-flop d) number system

A multiplexer can be used primarily to

- a) implement Boolean functions b) store information c) reduce Boolean functions

d) act as driver to 7-segment display

A 4x1 multiplexer has how many data inputs?

- a) 4 b) 3 c) 2 d) 1

A 4x1 multiplexer has how many data outputs?

- a) 1 b) 2 c) 3 d) 4

A 4x1 multiplexer has how many select/control inputs?

- a) 2 b) 1 c) 4 d) 8

An 8x1 multiplexer has how many data inputs?

- a) 8 b) 4 c) 2 d) 1

An 8x1 multiplexer has how many data outputs?

- a) 1 b) 2 c) 4 d) 8

An 8x1 multiplexer has how many select/control inputs?

- a) 3 b) 1 c) 4 d) 8

A demultiplexer has the same architecture as a

- a) decoder b) multiplexer c) encoder d) adder

A 1x4 demultiplexer has how many data inputs?

- a) 1 b) 2 c) 3 d) 4

A 1x4 demultiplexer has how many data outputs?

- a) 4 b) 3 c) 2 d) 1

A 1x4 demultiplexer has how many select/control inputs?

- a) 2 b) 1 c) 4 d) 8

A 4-bit adder device is also called a(n)

- a) ripple adder b) multiplexed adder c) serial adder d) complex adder

A 4-bit adder chip is internally composed of

- a) full-bit adders b) half-adders c) decoders d) multiplexers

The technique used to increase the speed of a 4-bit adder device is called

- a) lookahead carry b) overflow c) carry bit d) integration by parts

In a digital multiplication circuit, the component used to multiply two bits together is a(n)

- a) AND gate b) OR gate c) NAND gate d) XOR gate


The components of a combinational multiplication circuit primarily consist of

- a) AND gates and adders b) OR gates and decoders c) XOR gates and multiplexers
d) NAND gates and encoders

An ALU MSI device is a(n)

 
- a) arithmetic logic unit b) adder logic unit c) asynchronous logic unit d) average level unit

What outputs are generated by the decoder circuit below?



 
- a) D0=1, D1=0, D2=0, D3=0, D4=0, D5=0, D6=0, D7=0
b) D0=0, D1=0, D2=0, D3=0, D4=0, D5=0, D6=0, D7=0
c) D0=1, D1=1, D2=1, D3=1, D4=1, D5=1, D6=1, D7=1
d) D0=0, D1=1, D2=1, D3=1, D4=1, D5=1, D6=1, D7=1

What outputs are generated by the decoder circuit below?



 
- a) D0=0, D1=0, D2=0, D3=0, D4=0, D5=0, D6=1, D7=0
b) D0=0, D1=0, D2=0, D3=1, D4=0, D5=0, D6=0, D7=0
c) D0=0, D1=0, D2=1, D3=1, D4=0, D5=0, D6=0, D7=0
d) D0=1, D1=1, D2=1, D3=0, D4=1, D5=1, D6=1, D7=1
e) D0=1, D1=1, D2=1, D3=1, D4=1, D5=1, D6=0, D7=1

What outputs are generated by the decoder circuit below?



 
- a) D0=0, D1=0, D2=0, D3=1, D4=0, D5=0, D6=0, D7=0
- b) D0=0, D1=0, D2=0, D3=1, D4=0, D5=0, D6=0, D7=0
- c) D0=0, D1=0, D2=0, D3=1, D4=0, D5=0, D6=1, D7=0
- d) D0=1, D1=1, D2=1, D3=0, D4=1, D5=1, D6=1, D7=1
- e) D0=1, D1=1, D2=1, D3=0, D4=1, D5=1, D6=1, D7=1

What outputs are generated by the decoder circuit below?



 
- a) D0=0, D1=1, D2=1, D3=1, D4=1, D5=1, D6=1, D7=1
- b) D0=0, D1=0, D2=0, D3=0, D4=0, D5=0, D6=0, D7=0
- c) D0=1, D1=1, D2=1, D3=1, D4=1, D5=1, D6=1, D7=1
- d) D0=1, D1=0, D2=0, D3=0, D4=0, D5=0, D6=0, D7=0

What outputs are generated by the decoder circuit below?



 
- a) D0=1, D1=1, D2=1, D3=1, D4=1, D5=1, D6=0, D7=1
- b) D0=1, D1=1, D2=1, D3=0, D4=1, D5=1, D6=1, D7=1
- c) D0=1, D1=1, D2=1, D3=1, D4=1, D5=1, D6=1, D7=1
- d) D0=0, D1=0, D2=0, D3=0, D4=0, D5=0, D6=1, D7=0

What outputs are generated by the decoder circuit below?



 
- a) D0=1, D1=1, D2=1, D3=0, D4=1, D5=1, D6=1, D7=1
- b) D0=1, D1=1, D2=1, D3=1, D4=1, D5=1, D6=0, D7=1
- c) D0=1, D1=1, D2=1, D3=1, D4=1, D5=1, D6=1, D7=1
- d) D0=0, D1=0, D2=0, D3=0, D4=0, D5=0, D6=1, D7=0

What function is implemented by the decoder circuit below?



 
- a) $F(A,B,C) = \sum m(0, 1, 5)$ b) $F = 0$ c) $F = 1$ d) $F(A,B,C) = \sum m(1, 2, 6)$

What function is implemented by the circuit below?



 
- a) $F(A,B,C) = \sum m(0, 4, 5)$ b) $F = 0$ c) $F = 1$ d) $F(A,B,C) = \sum m(0, 1, 5)$

What function is implemented by the circuit below?



 
- a) $F = 1$ b) $F(A,B,C) = \sum m(0, 1, 5)$ c) $F = 0$ d) $F(A,B,C) = \sum m(2,3,4,6,7)$

What function is implemented by the circuit below?



 
- a) $F(A,B,C) = \sum m(0, 1, 5)$ b) $F = 0$ c) $F = 1$ d) $F(A,B,C) = \sum m(2,3,4,6,7)$

What function is implemented by the circuit below?



 
- a) $F = 0$ b) $F(A,B,C) = \sum m(0, 1, 5)$ c) $F = 1$ d) $F(A,B,C) = \sum m(2,3,4,6,7)$

What function is implemented by the multiplexer circuit below?



 
- a) $F(A,B) = \sum m(1, 2)$ b) $F(A,B) = \sum m(0, 3)$ c) $F = 0$ d) $F = 1$

What function is implemented by the circuit below?



 
- a) $F(A,B,C) = \sum m(0,3,6,7)$ b) $F(A,B,C) = \sum m(0, 1)$ c) $F = 0$ d) $F = 1$

What function is implemented by the circuit below?



 
- a) $F(A,B,C) = \sum m(1,2,6,7)$ b) $F(A,B,C) = \sum m(0,1,2)$ c) $F = 0$ d) $F = 1$

What function is implemented by the circuit below?



 
- a) $F(A,B,C) = \sum m(2,3,4,7)$ b) $F(A,B,C) = \sum m(1,2,6,7)$ c) $F = 0$ d) $F = 1$

What function is implemented by the circuit below?




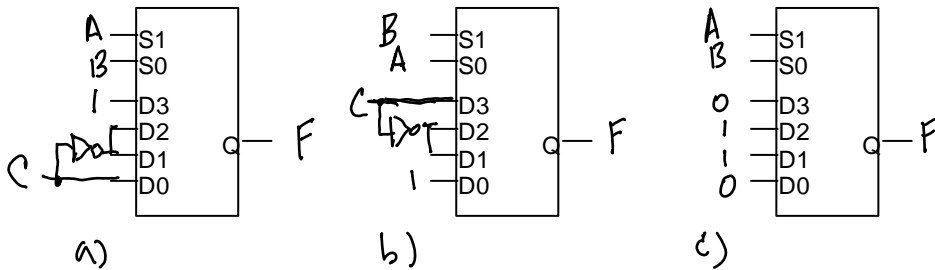- a) $F = 0$ b) $F = \sum m(1,2,6,7)$ c) $F = \sum m(0,1,2)$ d) $F = 1$


-- Implement the function $F(A,B,C) = \sum m(1,2,4,6,7)$ on a 4x1 MUX



 
-- Implement the function $F(A,B,C) = \sum m(1,2,4,6,7)$ on a 8x1 MUX



 
Implement the function $F(A,B,C) = \sum m(1,2,4)$ on a 3x8 Decoder



a)

 


b)

 


c)

 
Implement the function $F(A,B,C) = \sum m(1,2,4)$ on a 3x8 Decoder



a)

 


b)

 

c)

 What are the outputs of the following 4-bit adder circuit?




a) $C_{out} = 0$; $S_3=0$; $S_2=0$; $S_1=1$; $S_0=0$

b) $C_{out} = 0$; $S_3=0$; $S_2=0$; $S_1=1$; $S_0=1$

c) $C_{out} = 1$; $S_3=0$; $S_2=0$; $S_1=1$; $S_0=0$

 
d) $C_{out} = 1$; $S_3=0$; $S_2=0$; $S_1=1$; $S_0=1$

What are the outputs of the following adder circuit?



 - a) $C_{out} = 0; S_3=0; S_2=0; S_1=1; S_0=1$ b) $C_{out} = 0; S_3=0; S_2=0; S_1=1; S_0=0$
 c) $C_{out} = 1; S_3=0; S_2=0; S_1=1; S_0=1$ d) $C_{out} = 1; S_3=0; S_2=0; S_1=1; S_0=0$

What are the outputs of the following adder circuit?



- a) $C_{out} = 1; S_3=1; S_2=1; S_1=1; S_0=0$ b) $C_{out} = 1; S_3=1; S_2=1; S_1=1; S_0=1$
 c) $C_{out} = 1; S_3=0; S_2=0; S_1=1; S_0=0$ d) $C_{out} = 1; S_3=0; S_2=0; S_1=1; S_0=1$

How many outputs are required for a circuit that multiplies 2, 2-bit numbers?

- a) 4 b) 2 c) 3 d) 5 e) 6

How many outputs are required for a circuit that multiplies 2, 3-bit numbers?

- a) 6 b) 2 c) 3 d) 4 e) 5

Part 2: Signed Number Systems

The value, -1, is represented in a 5-bit 1's complement system as

- a) 11110 b) 11111 c) 00001 d) 10001

The value, -1, is represented in a 5-bit signed-magnitude system as

- a) 10001 b) 11111 c) 11110 d) 00001

The value, -1, is represented in a 5-bit 2's complement system as

- a) 11111 b) 11110 c) 00001 d) 10001

The value, -1, is represented in a 5-bit 2's complement system in hex is

- a) 1F b) 1E c) 01 d) 11

The value, +3, is represented in a 5-bit 1's complement system as

- a) 00011 b) 00010 c) 10011 d) 10011

The value, +3, is represented in a 5-bit signed-magnitude system as

- a) 00011 b) 00010 c) 10011 d) 10011

The value, +3, is represented in a 5-bit 2's complement system as

- a) 00011 b) 00010 c) 10011 d) 10011

The value, -3, is represented in a 4-bit 1's complement system as

- a) 1100 b) 1011 c) 1101 d) 1001

The value, -3, is represented in a 4-bit signed-magnitude system as

- a) 1011 b) 1101 c) 1100 d) 1001

The value, -3, is represented in a 4-bit 2's complement system as

- a) 1101 b) 1100 c) 1011 d) 1001

The most positive value in a 4-bit, 2's complement signed number system is

- a) 7 b) 15 c) 16 d) 8

The most positive value in a 4-bit, 1's complement signed number system is

- a) 7 b) 15 c) 16 d) 8

The most positive value in a 4-bit, signed-magnitude number system is

- a) 7 b) 15 c) 16 d) 8

The most negative value in a 4-bit, 2's complement signed number system is

- a) -8; b) -7 c) -15 d) -16

The most negative value in a 4-bit, 1's complement signed number system is

- a) -7 b) -8 c) -15 d) -16

The most negative value in a 4-bit, signed-magnitude number system is

- a) -7 b) -8 c) -15 d) -16

The most positive value in a 5-bit, 2's complement signed number system is

- a) 15 b) 16 c) 7 d) 31

The most positive value in a 5-bit, 1's complement signed number system is

- a) 15 b) 16 c) 7 d) 31

The most positive value in a 5-bit, signed-magnitude number system is

- a) 15 b) 16 c) 7 d) 31

The most negative value in a 5-bit, 2's complement signed number system is

- a) -16 b) -15 c) -8 d) -7

The most negative value in a 5-bit, 1's complement signed number system is

- a) -15 b) -16 c) -8 d) -7

The most negative value in a 5-bit, signed-magnitude number system is

- a) -15 b) -16 c) -8 d) -7

What is the binary representation of +10 in a 6-bit, 2's complement system?

- a) 001010 b) 110101 c) 1010 d) 110110

What is the binary representation of +10 in a 6-bit, 1's complement system?

- a) 001010 b) 110101 c) 1010 d) 110110

What is the hex representation of +10 in a 6-bit, 2's complement system?

- a) 0A b) 35 c) A d) 36

What is the binary representation of -10 in a 6-bit, 2's complement system?

- a) 110110 b) 110101 c) 111010 d) 101010

What is the hex representation of -10 in a 6-bit, 2's complement system?

- a) 36 b) 35 c) 3A d) 2A

What is the binary representation of -10 in a 6-bit, 1's complement system?

- a) 110101 b) 110110 c) 111010 d) 101010

What is the hex representation of -10 in a 6-bit, 1's complement system?

- a) 35 b) 36 c) 3A d) 2A

What is the binary representation of -10 in a 6-bit, signed+magn. complement system?

- a) 101010 b) 110110 c) 111010 d) 101011

What is the hex representation of -10 in a 6-bit, signed+magn. system?

- a) 2A b) 36 c) 3A d) 2B

Part 3: HDL

The term "HDL" means

- a) Hardware Description Language b) Hardware Description Laboratory
- c) Half-adder Decoder Logic d) Hardware Decoder Language

What does the term "VHDL" mean?

- a) VHSIC Hardware Description Language
- b) Very High Speed Design Language
- c) Very High Speed Design Laboratory
- d) VHSIC Hardware Description Laboratory

The term "ASIC" means

- a) Application Specific Integrated Circuit
- b) Application Speed Integrated Circuit
- c) Assisted Specific Integrated Circuit
- d) Auxiliary Sector Integrated

Which of the following is not a HDL?


- a) MultiSim b) VHDL c) Verilog

MultiSim simulation software primarily supports

- a) schematics capture b) VHDL c) ABEL d) Verilog

 
Part 4: RS (NAND and NOR) Latches

Given the latch circuit below, what are the outputs Q and Q'?



 - a) $Q=1, Q'=0$ b) $Q=1, Q'=1$ c) $Q=0, Q'=0$ d) $Q=0, Q'=1$ e) cannot be determined

Given the latch circuit below, what are the outputs Q and Q'?



- a) $Q=0, Q'=1$ b) $Q=0, Q'=0$ c) $Q=1, Q'=0$ d) $Q=1, Q'=1$ e) cannot be determined

Given the latch circuit below and the inputs R and S, determine output Q waveform

